

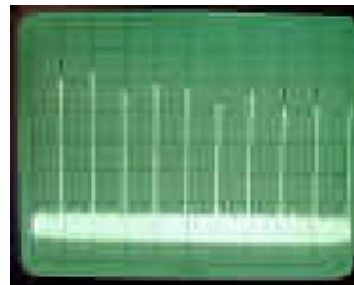



This signal source features a minimum-tune design. The only tuning necessary is the crystal oscillator trimmer and the interdigital filter. The crystal used here is a standard 5th overtone series-resonant AT cut; I chose 100.25444 so that the 9th harmonic would fall on 902.290. The oscillator actually overdrives the first MMIC, creating a harmonic-rich output, which is further enhanced by the 1N4148 multiplier diode. After passing through the interdigital filter, the 900 MHz signal is amplified to +10 dbm by the next 2 MMIC's.

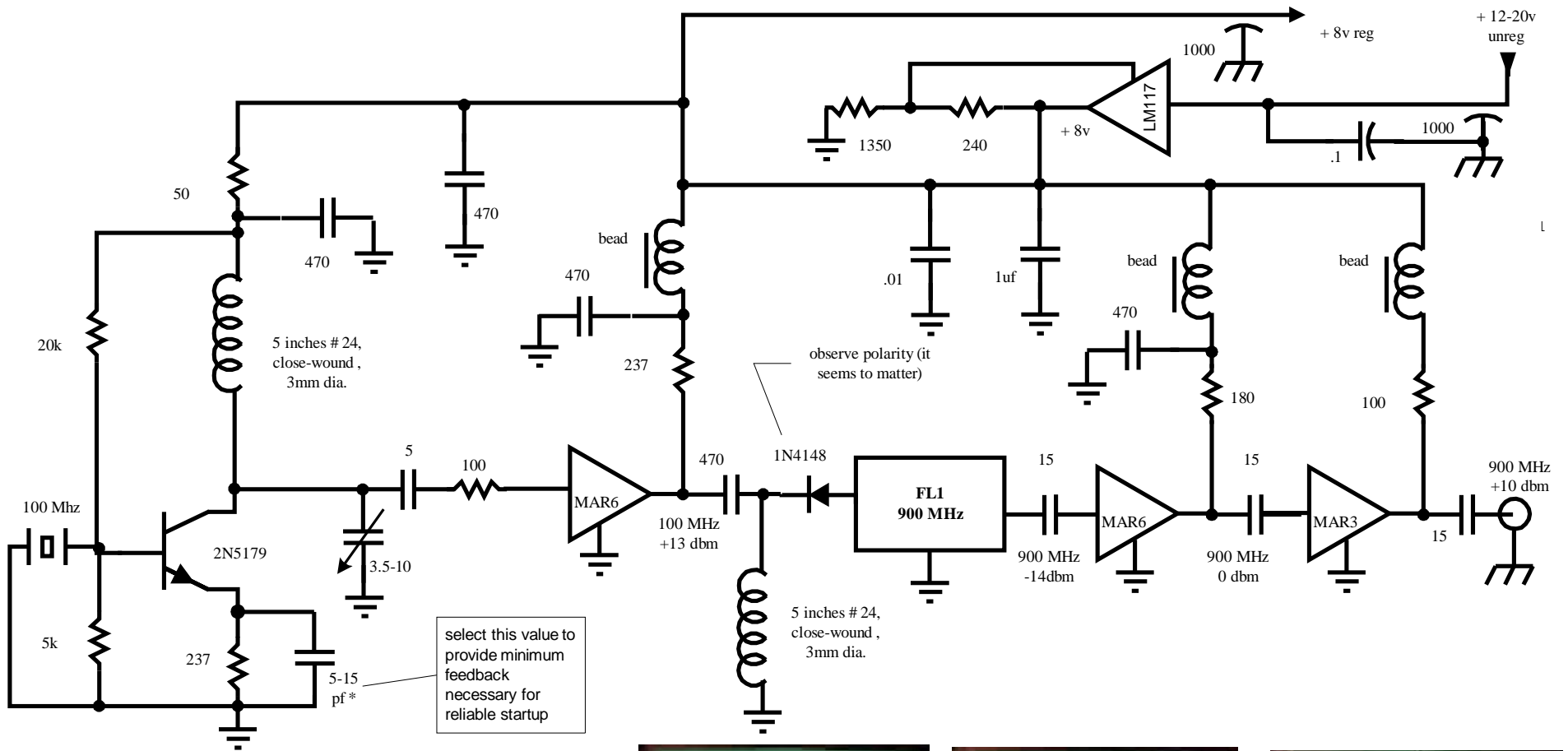

diode output comb

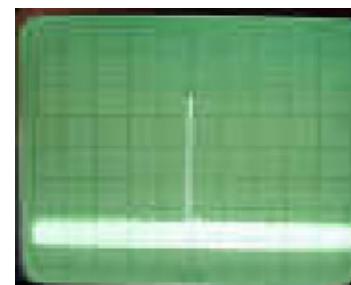

filtered 900 MHz

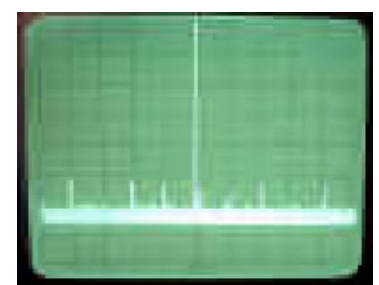

10 mw output